

Two-port Networks

Laboratory V

Patrycja Nazim, Adrian Król, Gabriel Ćwiek, Kamil Chaj

1 Goal of the exercise

The aim of this exercise is to familiarize with experimental methods of determining two-port network parameters by measuring output and input voltages and currents, and then compare theoretical and experimental results

2 Two-port networks

Two-port network can be regarded as "black box" with its properties specified by a characteristic matrix. It allows us to simplify large circuit with those "black boxes" and move to higher level of abstraction, instead of using simple passive element now we can using complex circuits but seeing them as simple 2×2 matrix similar to one in eq. (1).

$$\mathbf{Z} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \quad (1)$$

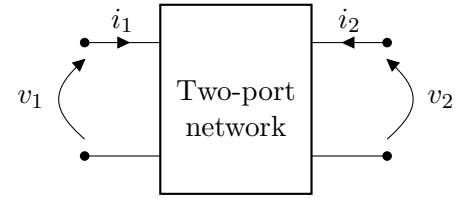


Figure 1: Two-port diagram

Characteristic matrix can have form of impedance \mathbf{Z} , admittance \mathbf{Y} or chain(ABCD) matrix and many more forms which we are not going to use during this exercise.

3 Course of measurements

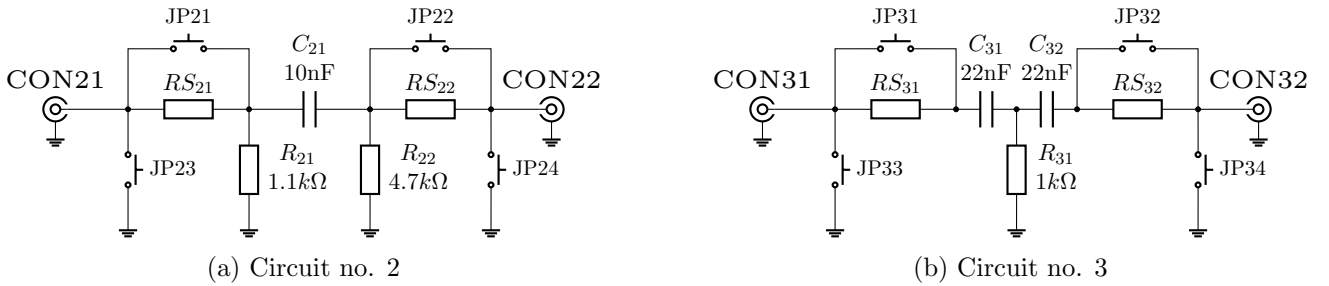


Figure 2: Measured circuits

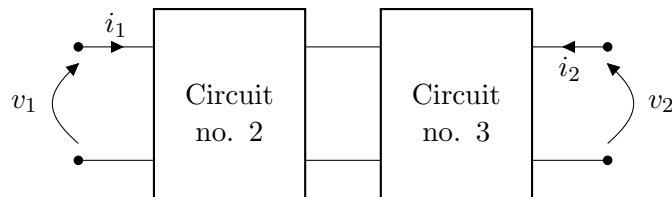


Figure 3: Chain configuration

4 Theoretical calculations

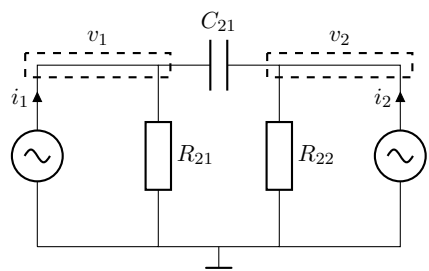


Figure 4: Simplified circuit no. 2

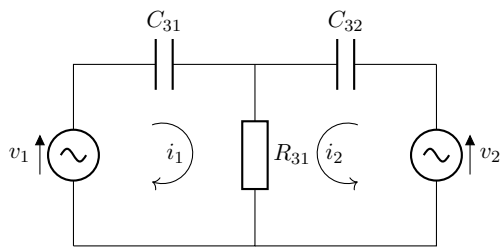


Figure 5: Simplified circuit no. 3

5 Comparison

6 Conclusions