

# Frequency Response Measurements

## Laboratory IV

Patrycja Nazim, Adrian Król, Gabriel Ćwiek, Kamil Chaj

- 1 Goal of the exercise
- 2 Frequency response
- 3 Course of measurements

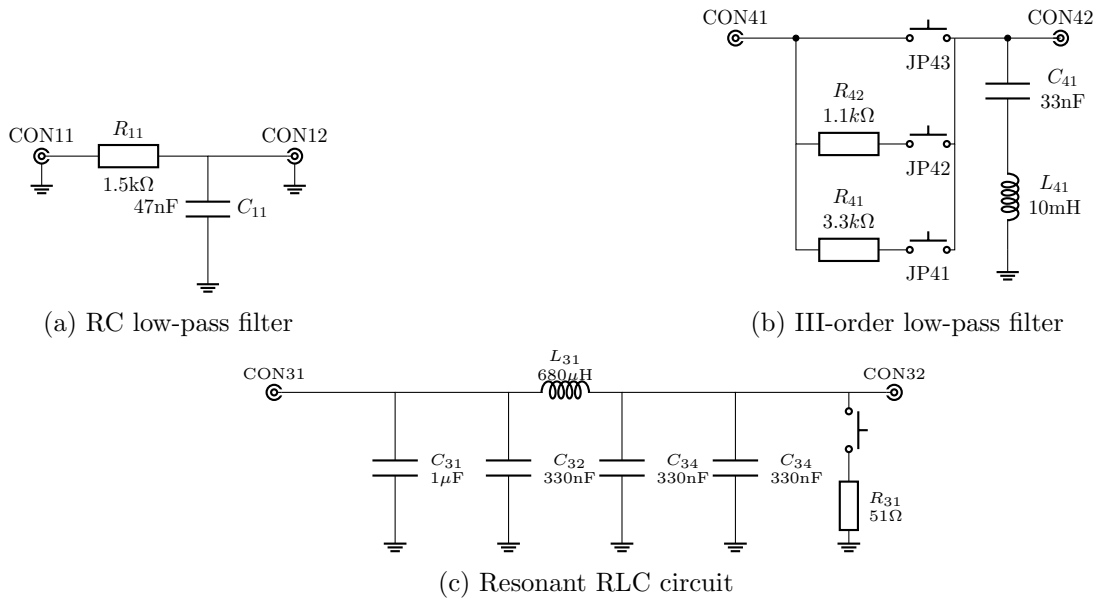


Figure 1: Measured circuits

## 4 Data processing

Source code for this section can be found in Appendix A

First step in finding amplitude-frequency characteristics was calculating gain in Volts

$$\text{Voltage gain [V]} = \frac{V_{\text{CON2}}}{V_{\text{CON1}}} \quad (1)$$

then we calculated voltage gain in decibels

$$\text{Voltage gain [dB]} = 20 \log_{10}(V_{\text{gain}}) \quad (2)$$

Voltage gain is on the left plot in figure 2, vertical blue axis represents scale in volts and orange axis decibel scale.

Phase-frequency characteristics didn't require any calculation and is simply plotted on the right plot in figure 2.



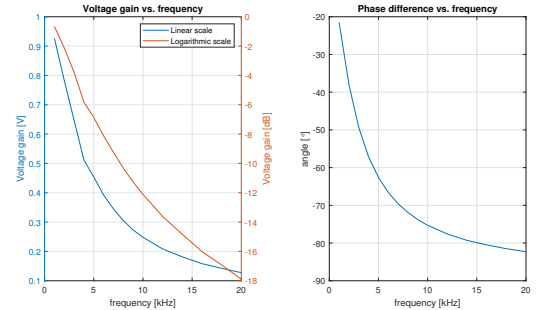
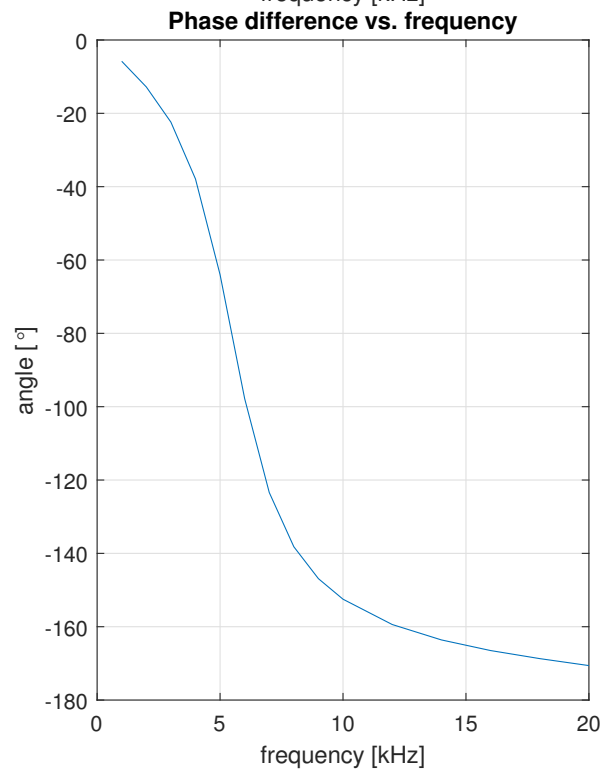
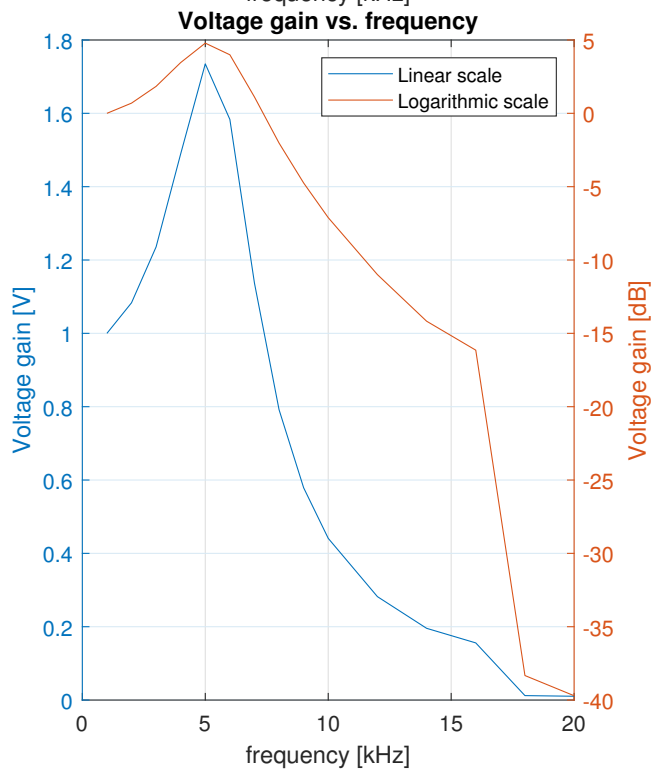
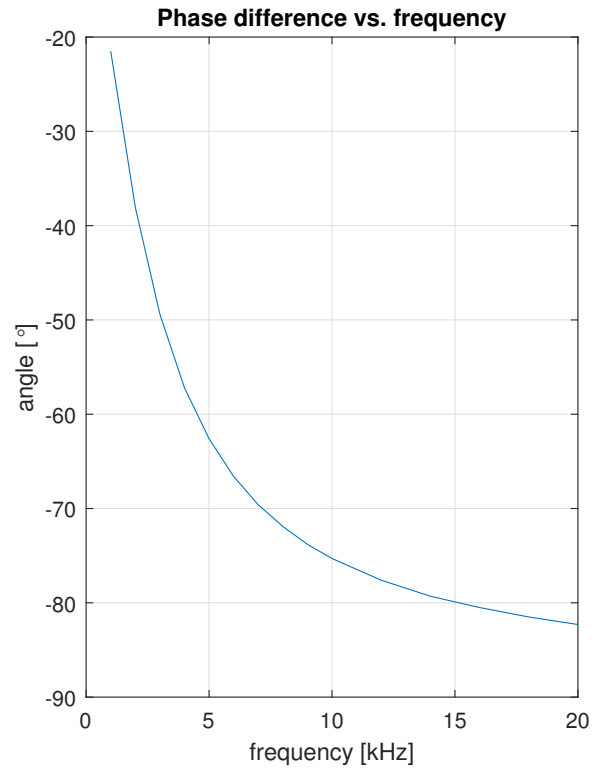
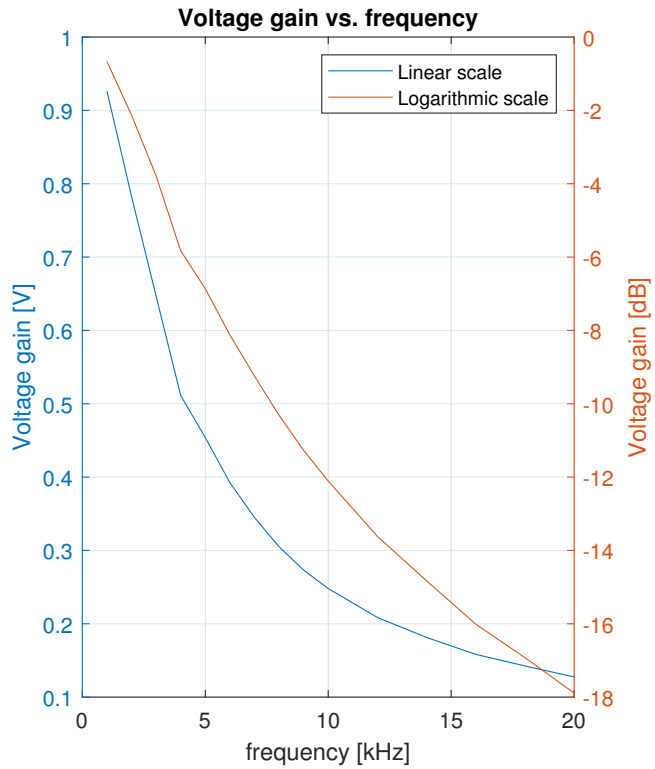
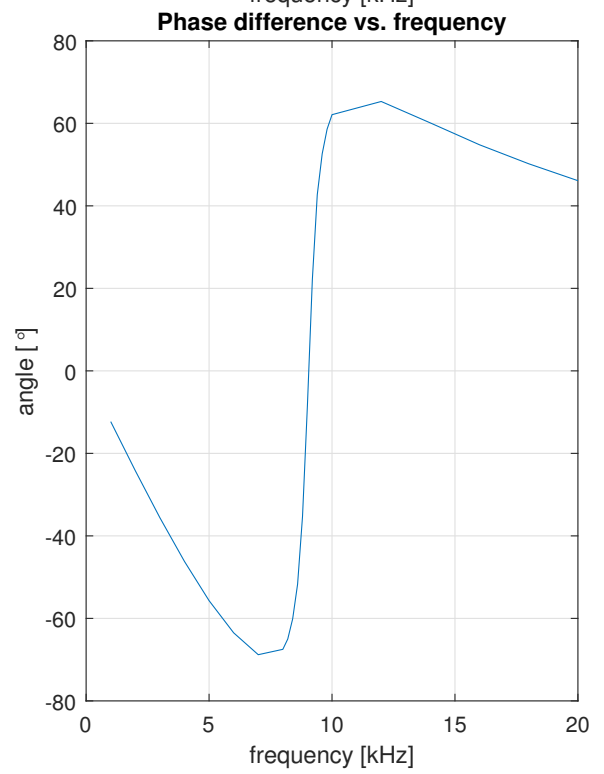
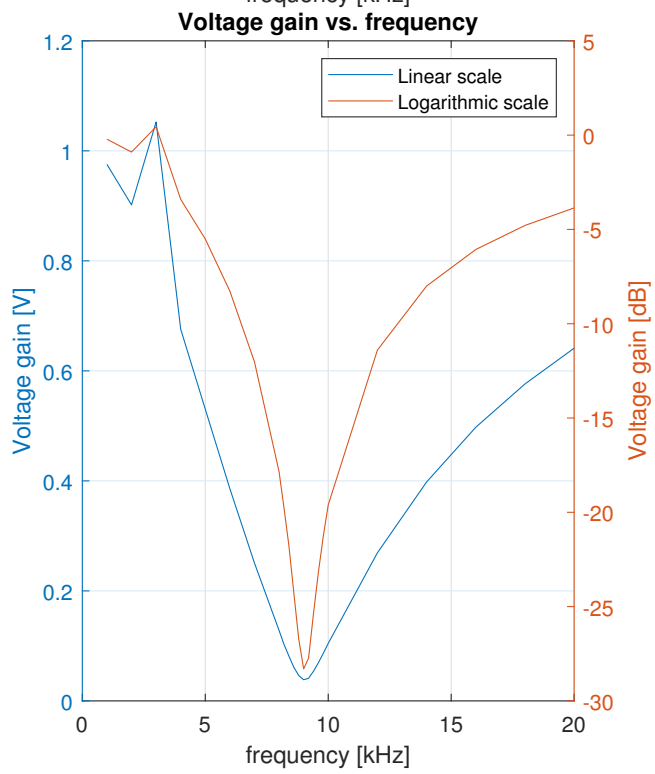


Figure 2: Example

## 5 Characteristics analysis

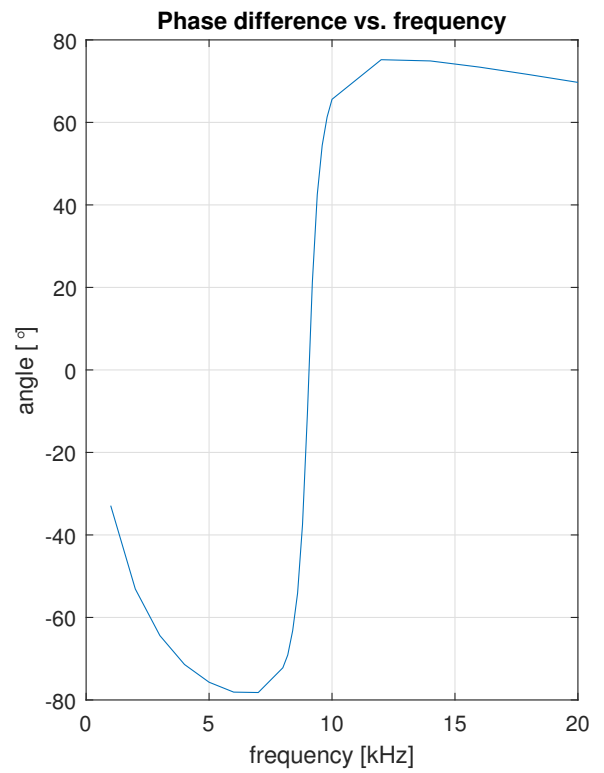

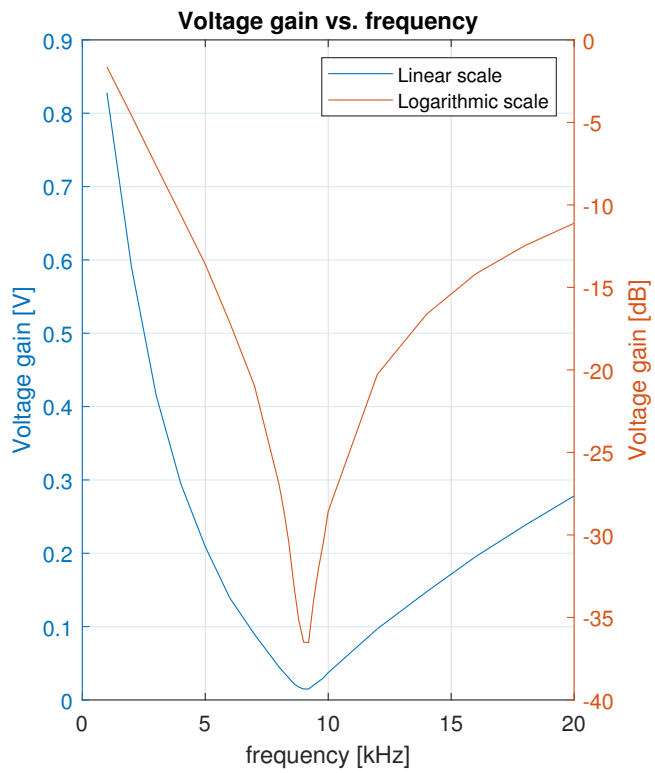

## 6 Conclusions

## A Appendix