

Laplace Transform

Laboratory III

Patrycja Nazim, Adrian Król, Gabriel Ćwiek, Kamil Chaj

- 1 Goal of the exercise
- 2 Laplace Transform
- 3 Course of measurements

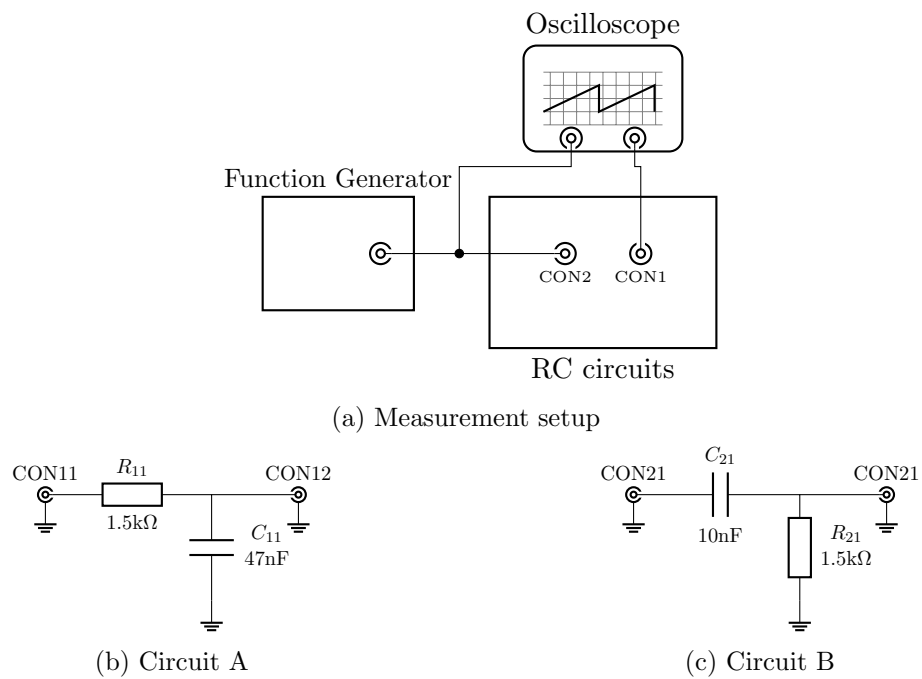


Figure 1: RC Circuits

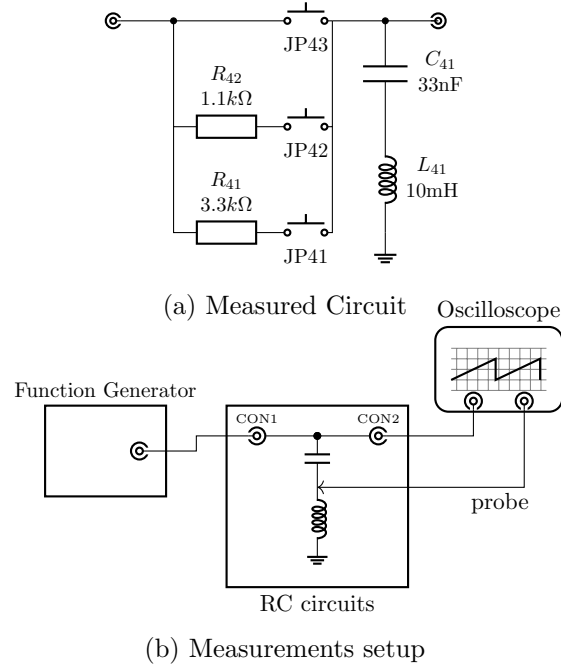


Figure 2: RLC circuit

4 Theoretical calculations

For all calculations we used Matlab with Symbolic Math Toolbox. Source code can be found in Appendix. A

In all three circuit input voltage was square wave with 50% duty cycle which can be described in time domain by

$$v_{in}(t) = V_{offset}\mathbf{1}(t) + V_{pp}\mathbf{1}(t - \frac{T}{2}) - V_{pp}\mathbf{1}(t - T) \quad (1)$$

and after Laplace transform into frequency domain

$$V_{in}(s) = \mathcal{L}[v_{in}(t)] = \frac{V_{offset}}{s} + \frac{e^{-\frac{T}{2}s}}{s} - \frac{e^{-Ts}}{s} \quad (2)$$

4.1 Circuit A

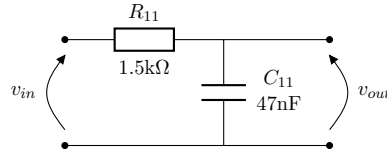


Figure 3: Circuit A schematics

v_{out} of circuit A can be described using simple voltage divider

$$v_{out}(s) = v_{in}(s) \frac{\frac{1}{sC_{11}}}{R_{11} + \frac{1}{sC_{11}}} \quad (3)$$

after applying inverse Laplace transform to $V_{out}(s)$ we obtain below plot.

Figure 4: Circuit A output voltage

4.2 Circuit B


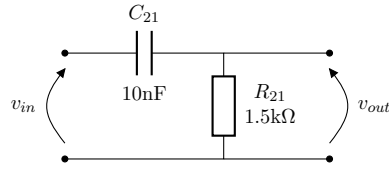


Figure 5: Circuit B schematics

4.3 Circuit C

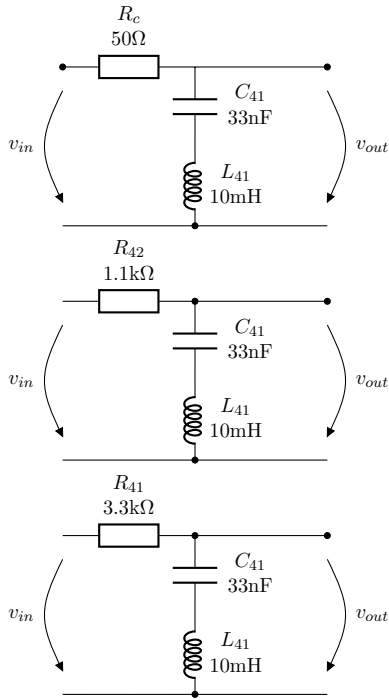

5 Comparison

6 Conclusions

A Appendix